

Please check that this question paper contains 09 questions and 02 printed pages within first ten minutes.

[Total No. of Questions: 09]

[Total No. of Pages: .....]

Uni. Roll No. ....

Program: B.Tech. (Batch 2018 onward)

MORNING

Semester: III

09 MAY 2023

Name of Subject: Electrical Circuit Analysis

Subject Code: PCEE-101

Paper ID: 16064

Scientific calculator is Allowed

Detail of allowed codes/charts/tables etc. ...Nil.

Time Allowed: 03 Hours

Max. Marks: 60.

**NOTE:**

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

**Part – A**

**[Marks: 02 each]**

**Q1.**

- a) Define a dependent voltage source with the help of a diagram.
- b) Describe unit ramp function and exponential function.
- c) Describe maximum power theorem.
- d) Calculate Laplace of  $\cos\omega t$ .
- e) Analyse series resonance.
- f) Determine the values of A,B,C,D for transmission parameters.

**Part – B**

**[Marks: 04 each]**


**Q2.** Explain transfer function representation with the help of a suitable circuit. What is an ideal transformer.

**Q3.** Describe Initial and final value theorem of Laplace.

**Q4.** Interpret open circuit parameters in terms of short circuit parameters.

**Q5.** For the circuit shown determine Norton's equivalent circuit between output terminals AB.

MORNING  
09 MAY 2023

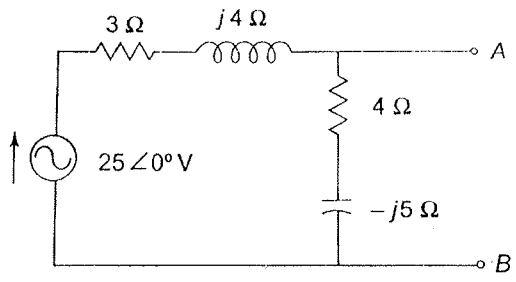

Q6. A 50Hz sinusoidal voltage  $v=311\sin\omega t$  is applied to a RL series circuit. If the magnitude of resistance is 5ohms and that of inductance is 0.02H. Evaluate the rms current, instantaneous current, voltage drop across resistor.

Q7. Evaluate Laplace inverse of  $\frac{4}{s^2+64}$

Part – C

[Marks: 12 each]

Q8. Solve for Step response of RL series circuit with appropriate circuit.

OR

Explain Superposition theorem, nodal analysis, Thevenin's theorem.

Q9. The driving point impedance of a LC network is represented by

$$Z(s) = 5 \frac{(s^2+4)(s^2+25)}{s(s^2+16)}$$

Evaluate First and Second form of foster

OR

The driving point impedance of a RC network is represented by

$$Z(s) = \frac{(s^2+5s+4)}{(s^2+2s)}$$

Evaluate First and Second form of Cauer

\*\*\*\*\*